

# **CSE260: Digital Logic Design**

**Project Title: Arithmetic Calculator**

**Group Number: 2**

**Members:**

**Jonathon Lenny Baroi - 20201013**

**Nafiun Al Amin - 20201069**

**Ajmain Mahtab - 20201034**

**Mashnoon Mayad - 20201033**

**Theory Section: 9**

## **Introduction and Objective**

No matter what degree one may be studying, one must always remember that Mathematics is a key component of everyday life. As such, an efficient way to calculate simple arithmetic operations is always of importance. A calculator allows us to do this, and using digital logic, we can create such a device. Our objective was to create a basic arithmetic calculator, with basic mathematical operations on two numbers.

## **Proposed Model:**

The calculator should be capable of three operations: addition, subtraction and multiplication.

The model for the calculator was split into a few parts. Firstly, an input system so that the user can decide if the user would like to add, subtract or multiply. The user can also input the numbers that he would like to operate on and the circuit would perform the selected operation.

Coming to the operations, for addition and subtraction, we created an 8 bit parallel adder cum subtractor for those two operations, which outputs an 8 bit number at maximum.

For multiplication, we created a 4 bit multiplier to multiply two 4 bit numbers and obtain a resultant 8 bit number.


There are additional displays to show the operands and the result in hexadecimal.

## Experimental Setup:

The components used in our circuit include:


- 7 segment BCD (Binary Coded Decimal) Display
- 4-bit binary Full Adders (74LS83)
- 8:4 Multiplexer (4019)
- AND gates
- LOGIC STATE
- XOR gates

**Figure 1: Main Circuit**

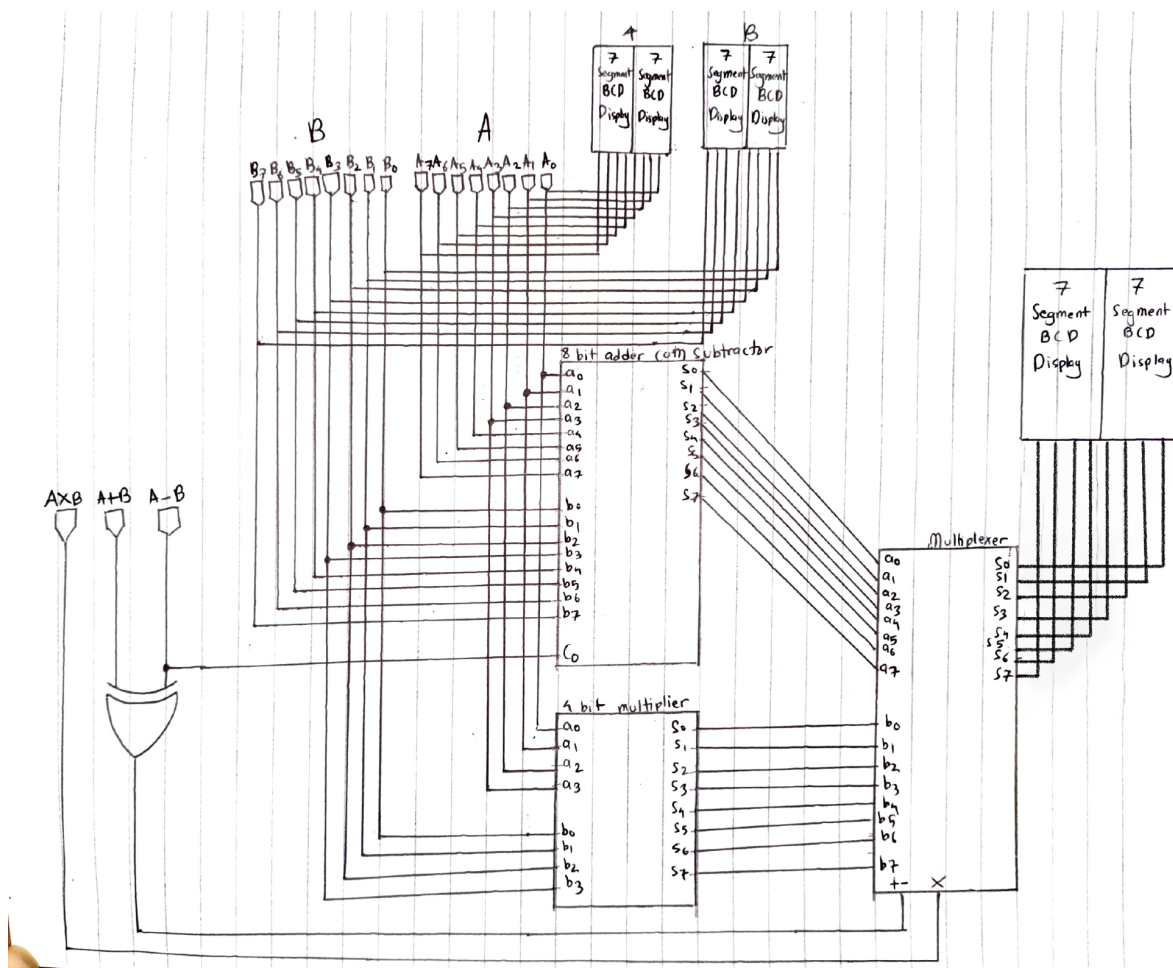

The LOGICSTATE has mainly been used to allow the user to input their values (in binary) into the calculator. It has also been used as a switch, to choose between different operations. Each of three LOGIC STATES control the operation, and each of them should only be HIGH while the others are LOW.


**Figure 2: 8 bit Full Adder cum Subtractor**

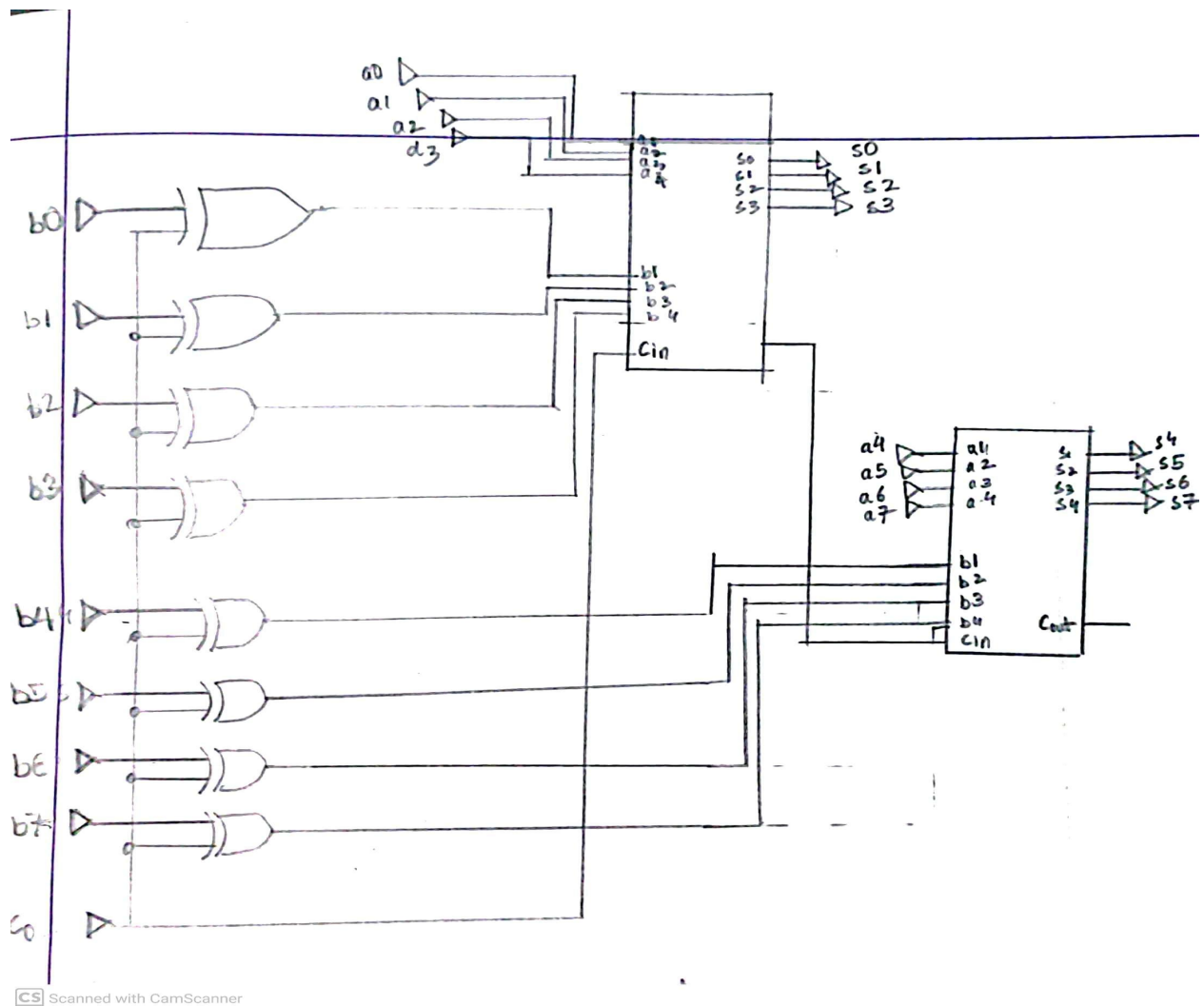

Two 4-bit full adders have been connected together to create one single 8 bit full adder cum subtractor . This is achieved by connecting the Carry-out (  $C_{out}$  ) of the first full adder with the Carry-in (  $C_{in}$  ) of the second full adder.


Alongside that, XOR gates have been added to the inputs to allow subtraction to take place, when needed. By default, with a  $C_{in}$  value of 0, the circuit performs 8 bit addition. However, if the user activates subtraction, the  $C_{in}$  is changed to 1 and the same circuit now performs 8 bit subtraction.

**Figure 3: 4 bit Multiplier**

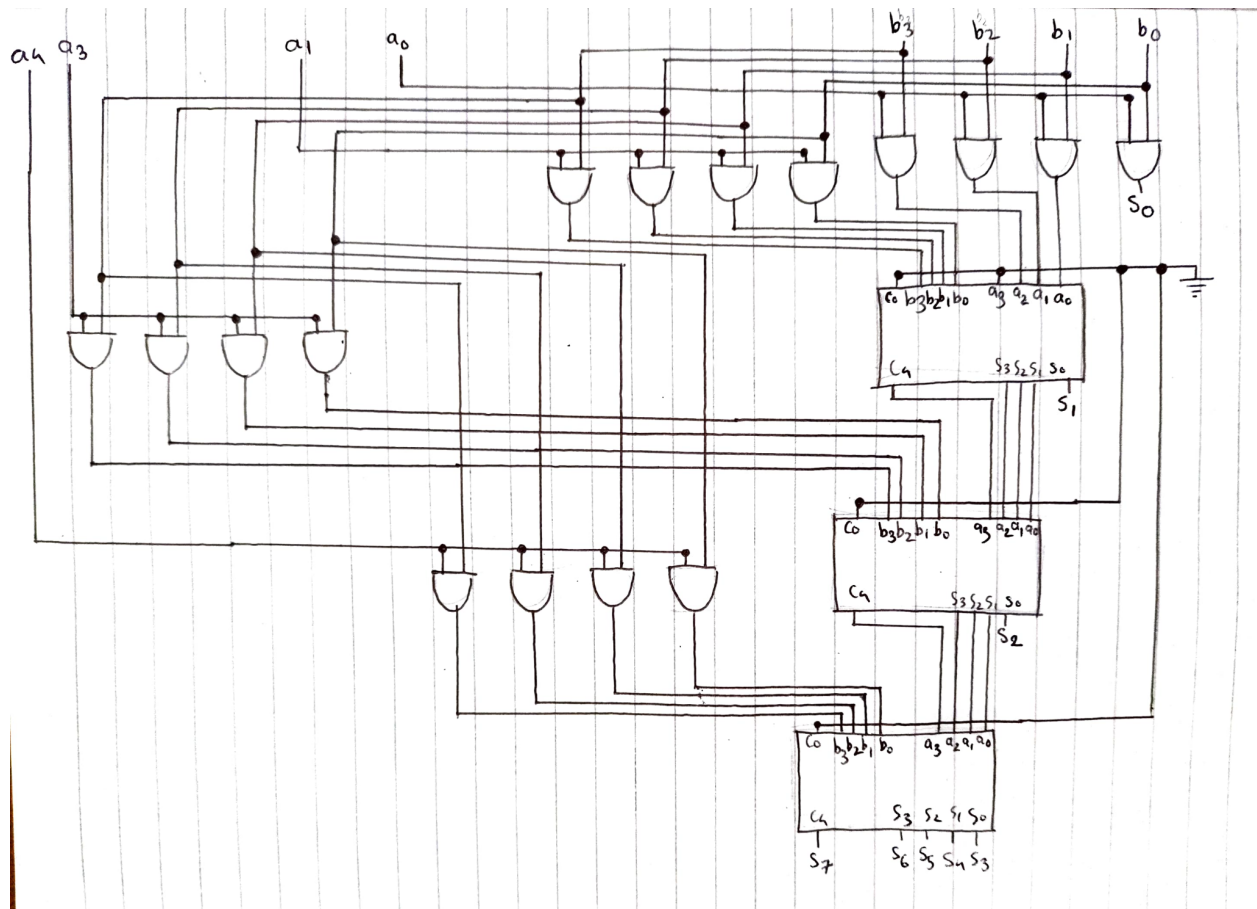

For multiplication of 4 bit numbers, 4 numbers are created using AND gates, which are the results of multiplication of the digits of one number with another. These numbers are then shifted accordingly to the left following the rules of multiplication, and then added using 4 bit adders. The result is an 8 bit number.

**Figure 4: 16 : 4 Multiplexer**

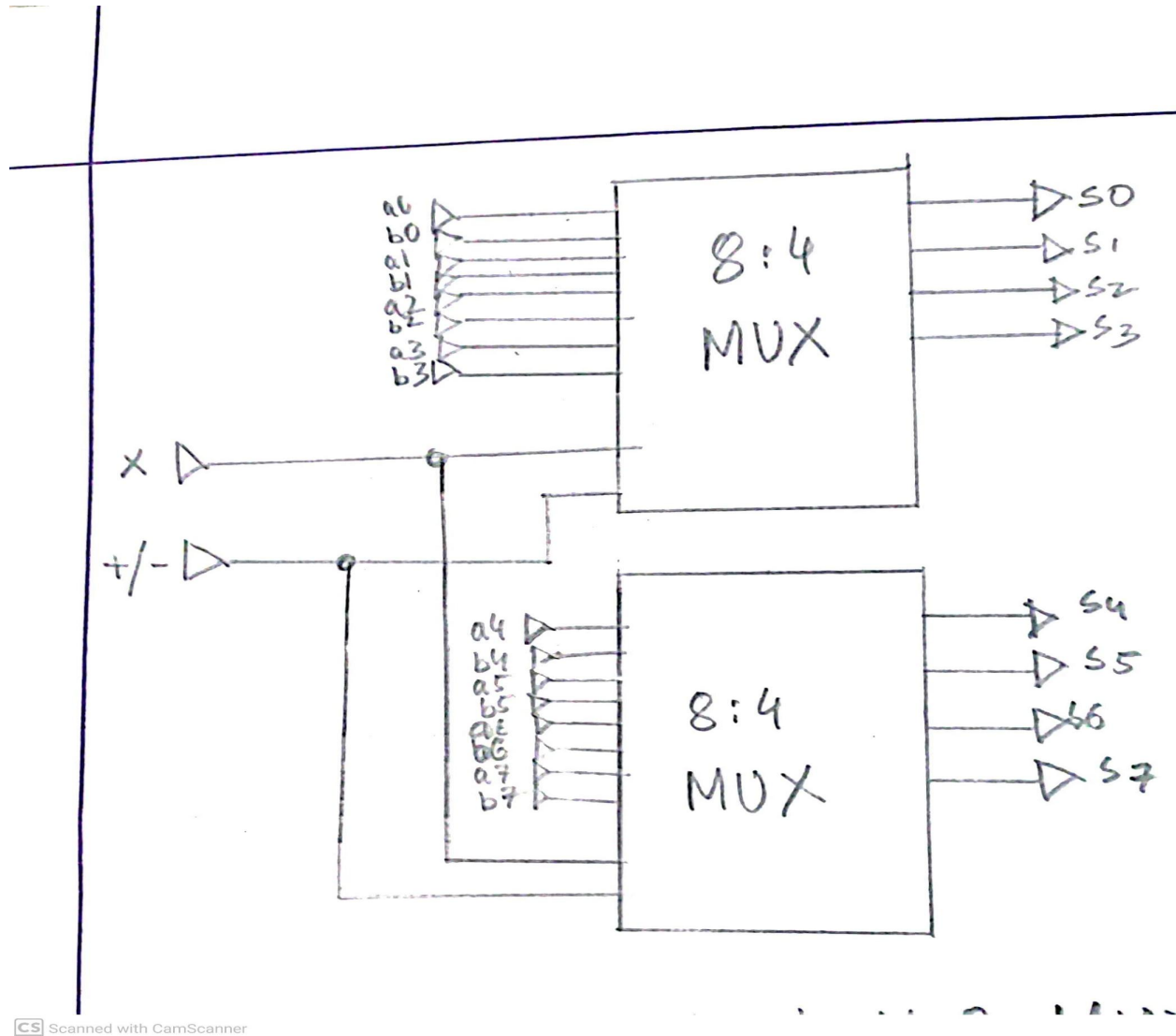

After calculation, the output of the adder/subtractor and multiplier is passed through a multiplexer. Depending on which operation was picked, the multiplexer outputs the value from that specific operation. For example, if addition was performed, only the output from the adder cum subtractor is considered and the subsequent output is returned.

Finally, the output goes through a 7 segment BCD display. The results of the binary operation are displayed in hexadecimal form, and the display offers a very discernible and easy to read output.

### Results and Analysis:

Op input				Input A									Input B									Output							
c	c	c		A	A	A	A	A	A	A		B	B	B	B	B	B	B		S	S	S	S	S	S	S			
0	1	2		7	6	5	4	3	2	1	0		7	6	5	4	3	2	1	0		7	6	5	4	3	2	1	0
0	0	1		0	0	0	0	1	1	1	1		0	0	0	0	1	1	1	1		1	1	1	0	0	0	0	1
0	0	1		0	0	0	0	0	0	0	0		0	0	0	0	0	0	0	0		0	0	0	0	0	0	0	0
0	0	1		0	0	0	0	0	1	0	0		0	0	0	0	0	0	0	1		0	0	0	0	1	0	0	0
0	0	1		0	0	0	0	0	1	0	1		0	0	0	0	1	0	1	0		0	1	1	0	0	1	0	0
0	0	1		0	0	0	0	1	0	0	1		0	0	0	0	1	0	0	1		0	1	0	1	0	0	0	1
0	0	1		0	0	0	0	1	1	0	0		0	0	0	0	1	1	0	0		1	0	0	1	0	0	0	0
0	0	1		0	0	0	0	1	0	1	1		0	0	0	0	1	0	1	1		0	1	1	1	1	0	0	1
0	0	1		0	0	0	0	0	0	0	1		0	0	0	0	0	0	0	1		0	0	0	0	0	0	0	1
0	1	0		0	0	0	0	0	0	0	0		0	0	0	0	0	0	0	0		0	0	0	0	0	0	0	0
0	1	0		1	1	1	1	1	1	1	1		1	1	1	1	1	1	1	1		1	1	1	1	1	1	1	0
0	1	0		1	0	1	0	1	0	1	0		1	0	1	0	1	0	1	0		0	1	0	1	0	1	0	0

Op input				Input A								Input B								Output							
0	1	0		1	1	1	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	0	0	0	0	0
0	1	0		0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1	0	0	0	1	1	1	1	0
0	1	0		0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1	0	1	1	0	0	1	1	0
0	1	0		0	0	0	1	1	1	0	0	0	0	0	1	1	1	0	0	0	0	1	1	1	0	0	0
0	1	0		1	1	1	0	0	0	1	1	1	1	1	0	0	0	1	1	1	0	0	0	1	1	0	0
1	0	0		1	1	1	0	0	0	1	1	1	1	1	0	0	0	1	1	0	0	0	0	0	0	0	0
1	0	0		1	1	1	0	0	1	1	0	1	0	1	0	1	0	1	0	0	0	1	1	0	0	0	0
1	0	0		1	1	1	1	1	1	1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
1	0	0		0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1	0	0	0	0	0	0	0	1
1	0	0		1	1	1	0	1	1	1	1	0	0	0	1	0	0	0	0	1	1	0	1	1	1	1	1
1	0	0		1	1	1	1	0	0	0	0	0	0	0	0	1	1	1	1	1	1	0	0	0	0	0	1
1	0	0		1	1	1	1	1	1	0	0	1	1	1	0	0	0	0	0	0	0	0	0	1	0	0	0
1	0	0		1	1	1	0	0	0	0	0	0	0	0	0	1	1	1	1	1	0	1	1	0	0	0	1

The operator inputs are c0, c1 and c2. These control which operations are being done. When only c0 is 1, input B is subtracted from A. When only c1 is



1, the inputs are added together. When only c2 is 1, input A and B are multiplied.

It is to be noted that during multiplication, the number being used as input should be a 4-bit number at maximum, so as to not exceed the output range of 8 bits when operated.

### **Conclusion:**

While the calculator can perform most arithmetic operations, **it cannot perform divisions**. It also displays the output in **hexadecimal**, and not decimal. **The multiplier also cannot take 8-bit inputs** like the adder/subtractor, and is limited to taking 4 bits, as multiplication of two 8-bit numbers would result in a 16-bit number, which is beyond the output range of the calculator.

For **subtraction**, negative results cannot be represented.

**It is to be noted that the selector also requires the user to have a HIGH input on the corresponding operation, and a low on the non-corresponding ones**; if not, the output does not match, but the output does not notify anything about the error. A low input on all 3 operator values also results in an error, where an output is still generated (given that a number is still being input).

Also, the input numbers have to be input in binary, **missing the user-friendliness** of a decimal **numpad** with numbers and operations.

